
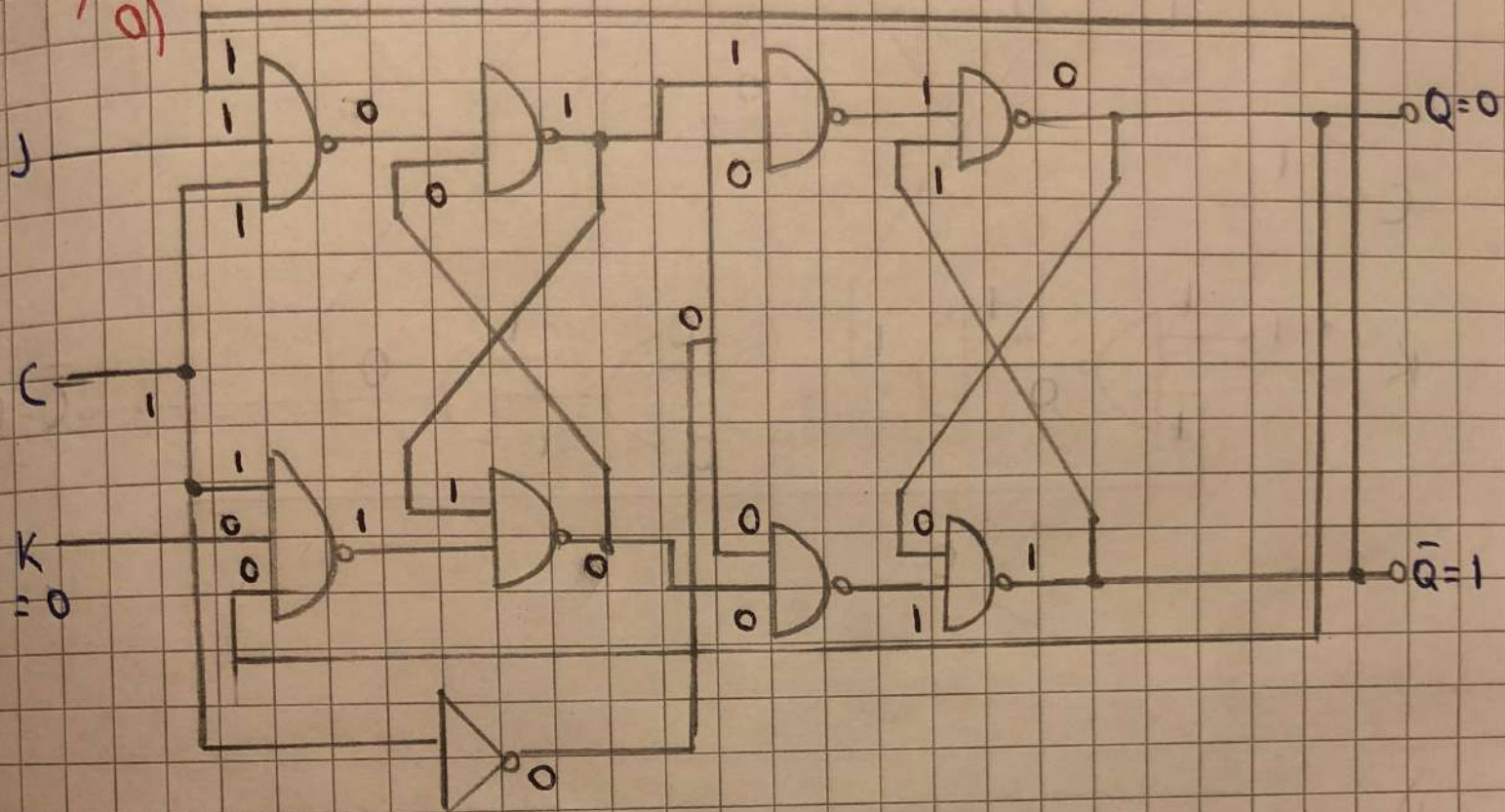




SHEET 9



1) a)

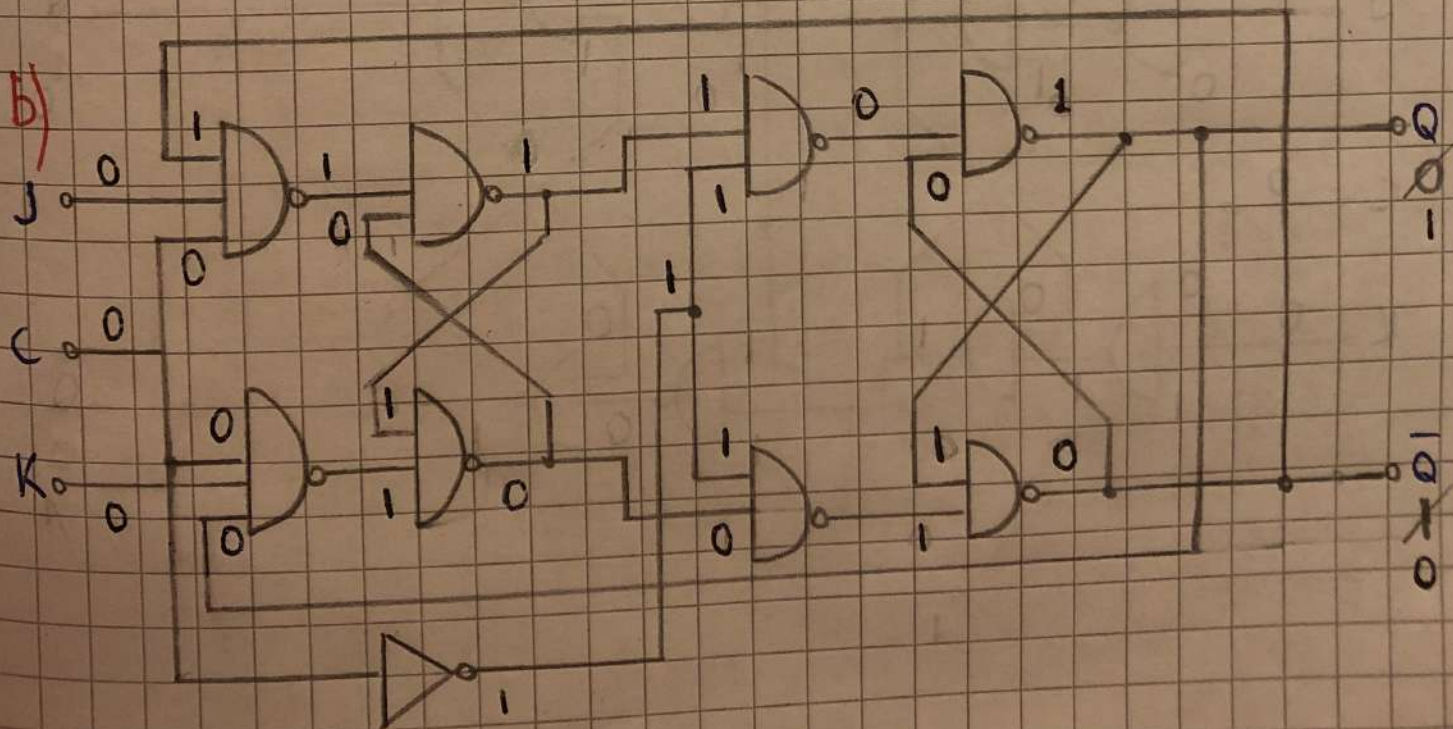

b)



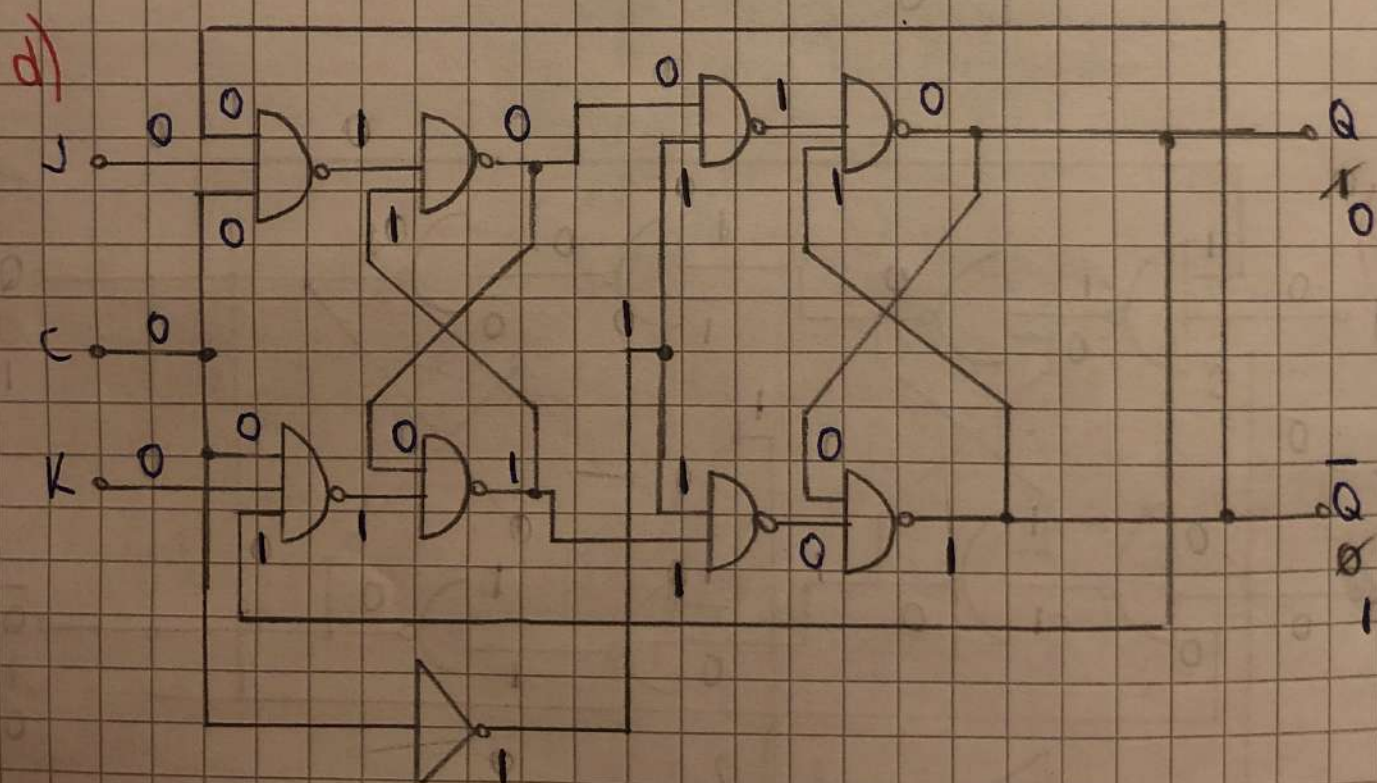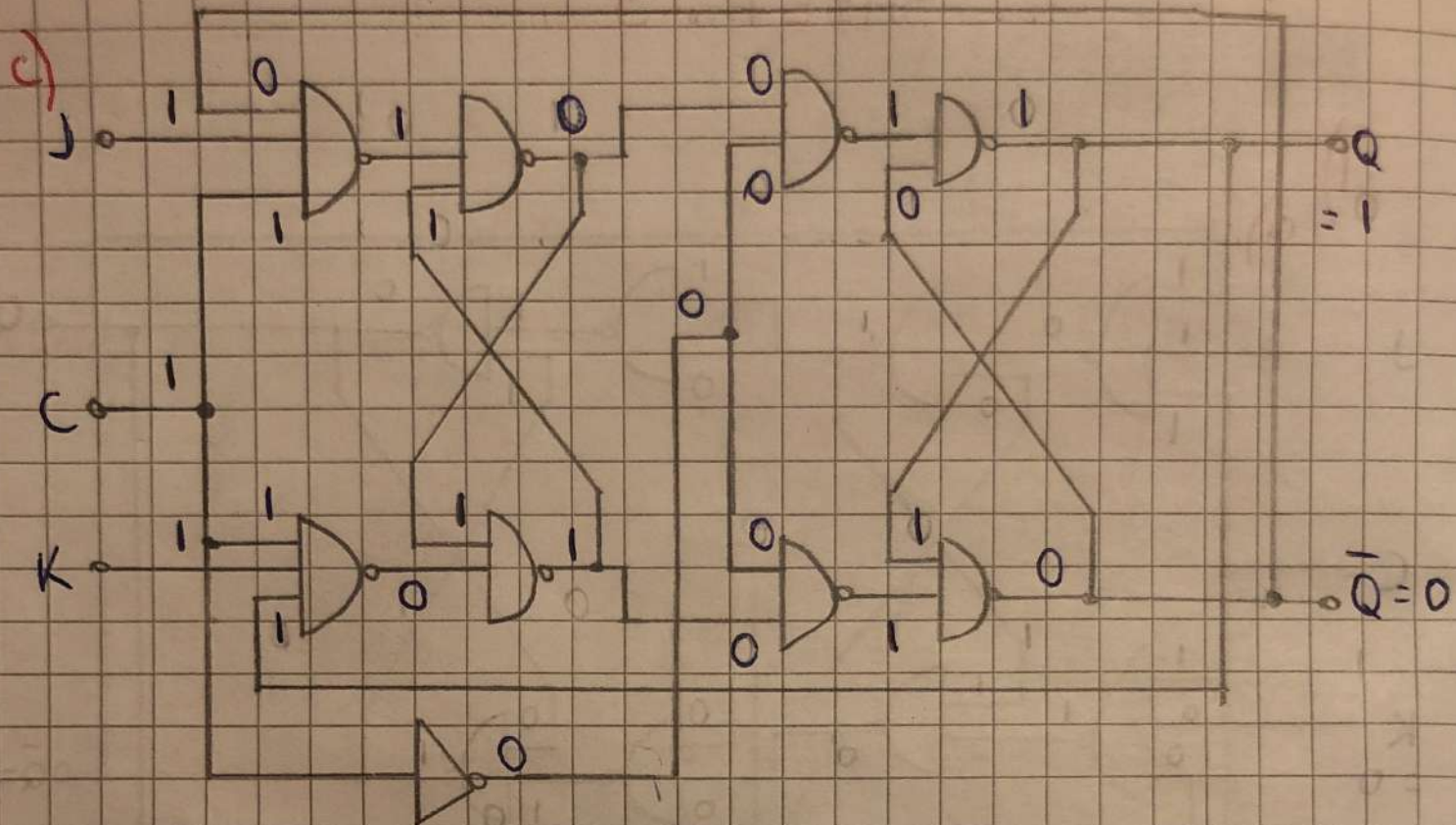

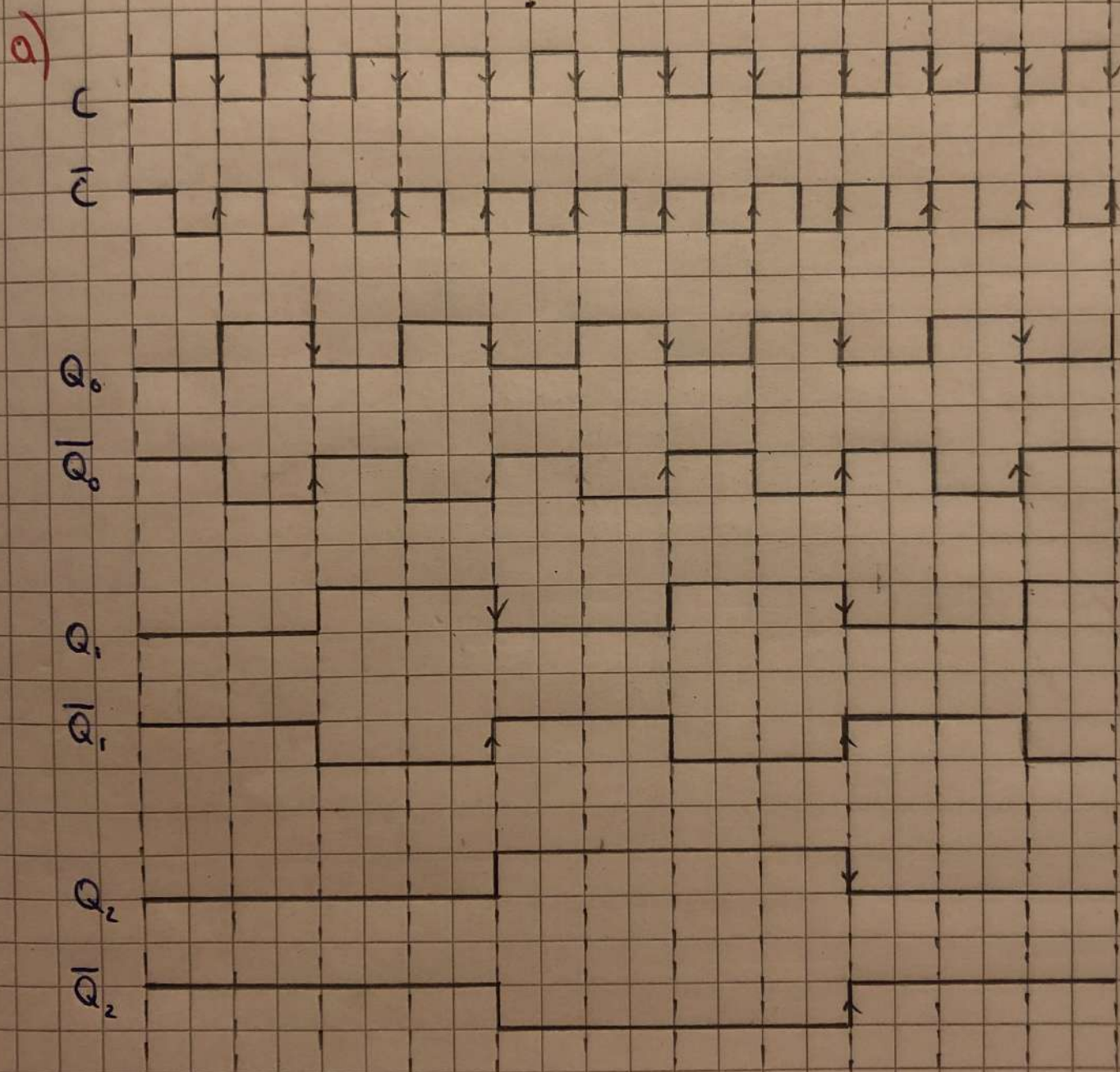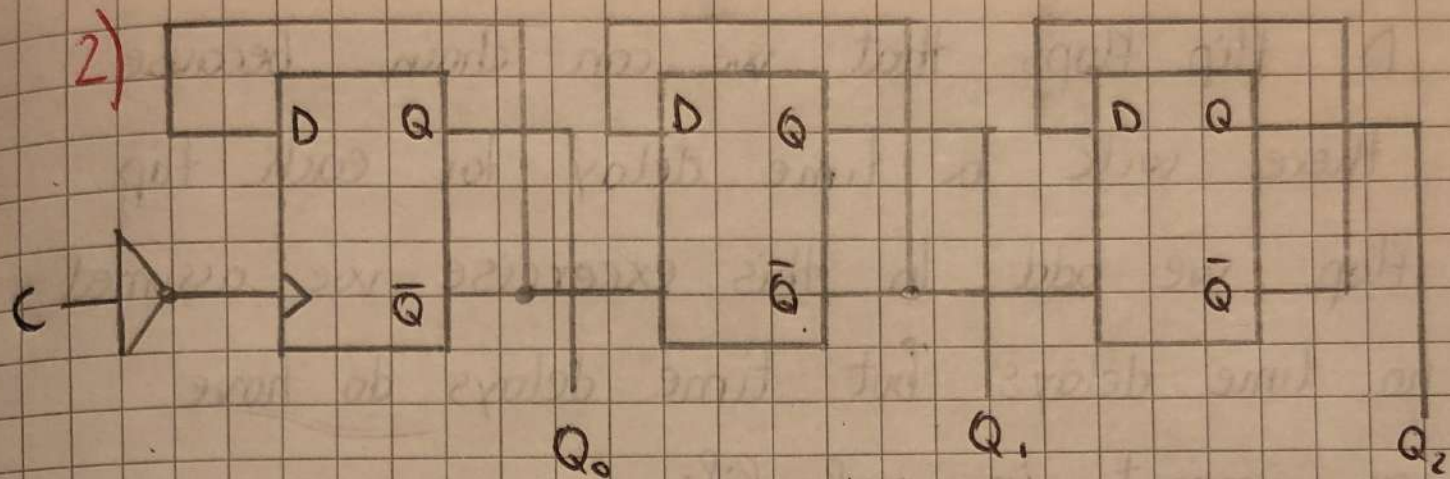

b) No, you can't make ripple counters arbitrary long. There is a limit on the number of

D flip flops that we can chain because there will a time delay for each flip flop we add. In this exercise we assumed no time delays but time delays do have an impact in real life.